

Fall 2020
California State University, Northridge
Department of Electrical and Computer Engineering
Computer Assignment 1: Design of a Combination Multiplier

Part I:

Half Adder Design (Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: ha - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13
14 -- Uncomment the following library declaration if using
15 -- arithmetic functions with Signed or Unsigned values
16 --use IEEE.NUMERIC_STD.ALL;
17
18 -- Uncomment the following library declaration if instantiating
19 -- any Xilinx leaf cells in this code.
20 --library UNISIM;
21 --use UNISIM.VComponents.all;
22
23 entity ha is
24     Port ( a : in STD_LOGIC;
25           b : in STD_LOGIC;
26           sum : out STD_LOGIC;
27           cout : out STD_LOGIC);
28 end ha;
29
30 architecture Behavioral of ha is
31
32     begin
33
34     sum <= a xor b;
35     cout <= a and b;
36
37 end Behavioral;
```

Half Adder Design (Test Bench Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: ha_tb - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity ha_tb is
16     -- Port ( );
17 end ha_tb;
18
19 architecture Behavioral of ha_tb is
20
21     signal a_tb: std_logic;
22     signal b_tb: std_logic;
23     signal sum_tb: std_logic;
24     signal cout_tb: std_logic;
25
26 component ha is
27     Port ( a : in STD_LOGIC;
28           b : in STD_LOGIC;
29           sum : out STD_LOGIC;
30           cout : out STD_LOGIC);
31 end component ha;
32
33 begin
34
35 uut: ha port map ( a => a_tb,
36                   b => b_tb,
37                   sum => sum_tb,
38                   cout => cout_tb);
39
40 process
41     begin
42
43     for aFor in 0 to 1 loop
44         for bFor in 0 to 1 loop
45
46             if aFor = 1 then a_tb <= '1';
47             else a_tb <= '0';
48             end if;
49
50             if bFor = 1 then b_tb <= '1';
51             else b_tb <= '0';
```

```

52 end if;
53
54 wait for 325ns;
55
56 end loop;
57 end loop;
58
59 end process;
60 end Behavioral;

```

Half Adder Design (Waveforms)



Full Adder Design (Code)

```

1 -----
2 -- Engineer: Jose Luis Martinez
3 --
4 -- Create Date: 09/14/2020 09:33:16 AM
5 -- Module Name: fa - Behavioral
6 -- Project Name: Computer Assignment 1
7 -- Revision 0.01 - File Created
8 -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13
14 entity fa is
15     Port ( a : in STD_LOGIC;
16           b : in STD_LOGIC;
17           cin : in STD_LOGIC;
18           sum : out STD_LOGIC;
19           cout : out STD_LOGIC);
20 end fa;
21
22 architecture Behavioral of fa is
23
24     begin
25
26     sum <= a xor b xor cin;
27     cout <= (a and b) or (a and cin) or (b and cin);
28
29 end Behavioral;
30

```

Full Adder Design (Test Bench Code)


```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: fa_tb - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity fas_tb is
16     -- Port ( );
17 end fas_tb;
18
19 architecture Behavioral of fas_tb is
20
21     signal a_tb: std_logic;
22     signal b_tb: std_logic;
23     signal cin_tb: std_logic;
24     signal sum_tb: std_logic;
25     signal cout_tb: std_logic;
26
27     component fa is
28         Port ( a : in STD_LOGIC;
29               b : in STD_LOGIC;
30               cin : in STD_LOGIC;
31               sum : out STD_LOGIC;
32               cout : out STD_LOGIC);
33     end component fa;
34
35     begin
36
37     uut: fa port map ( a => a_tb,
38                       b => b_tb,
39                       cin => cin_tb,
40                       sum => sum_tb,
41                       cout => cout_tb);
42
43     process
44     begin
45
46     for aFor in 0 to 1 loop
47         for bFor in 0 to 1 loop
48             for cinFor in 0 to 1 loop
49
50                 if aFor = 1 then a_tb <= '1';
51                 else a_tb <= '0';
52                 end if;
53
54                 if bFor = 1 then b_tb <= '1';
55                 else b_tb <= '0';
56                 end if;
```

```

57 :
58 ⊞      if cinFor = 1 then cin_tb <= '1';
59 :      else cin_tb <= '0';
60 ⊞      end if;
61 :      wait for 325ns;
62 :
63 ⊞      end loop;
64 ⊞      end loop;
65 ⊞ end loop;
66 :
67 ⊞ end process;
68 ⊞ end Behavioral;

```

Full Adder Design (Waveforms)

 

4x4 Multiplier Design (Code)

```

1 ⊞ -----
2 : -- Engineer: Jose Luis Martinez
3 : --
4 : -- Create Date: 09/14/2020 09:33:16 AM
5 : -- Module Name: mult4x4 - Behavioral
6 : -- Project Name: Computer Assignment 1
7 : -- Revision 0.01 - File Created
8 ⊞ -----
9 :
10 :
11 :
12 : library IEEE;
13 : use IEEE.STD_LOGIC_1164.ALL;
14 : use IEEE.NUMERIC_STD.ALL;
15 :
16 ⊞ entity mult4x4 is
17 :     Port ( x : in STD_LOGIC_VECTOR(3 downto 0);
18 :           y : in STD_LOGIC_VECTOR(3 downto 0);
19 :           p : out STD_LOGIC_VECTOR(7 downto 0));
20 ⊞ end mult4x4;
21 :
22 ⊞ architecture Behavioral of mult4x4 is
23 :
24 ⊞ component ha is
25 :     Port ( a : in STD_LOGIC;
26 :           b : in STD_LOGIC;
27 :           sum : out STD_LOGIC;
28 :           cout : out STD_LOGIC);
29 ⊞ end component ha;
30 :
31 ⊞ component fa is
32 :     Port ( a : in STD_LOGIC;

```



```

33         b : in STD_LOGIC;
34         cin : in STD_LOGIC;
35         sum : out STD_LOGIC;
36         cout : out STD_LOGIC);
37 end component fa;
38
39 signal x0y0, x0y1, x0y2, x0y3: std_logic;
40 signal x1y0, x1y1, x1y2, x1y3: std_logic;
41 signal x2y0, x2y1, x2y2, x2y3: std_logic;
42
43 signal x3y0, x3y1, x3y2, x3y3: std_logic;
44
45 signal c00, c01, c02, c03, c10, c11, c12, c13, c20, c21, c22, c23, c30, c31, c32, c33: std_logic;
46 signal s00, s01, s02, s03, s10, s11, s12, s13, s20, s21, s22, s23, s30, s31, s32, s33: std_logic;
47
48 begin
49     x0y0 <= x(0) and y(0);
50     x0y1 <= x(0) and y(1);
51     x0y2 <= x(0) and y(2);
52     x0y3 <= x(0) and y(3);
53     x1y0 <= x(1) and y(0);
54     x1y1 <= x(1) and y(1);
55     x1y2 <= x(1) and y(2);
56     x1y3 <= x(1) and y(3);
57     x2y0 <= x(2) and y(0);
58     x2y1 <= x(2) and y(1);
59     x2y2 <= x(2) and y(2);
60     x2y3 <= x(2) and y(3);
61     x3y0 <= x(3) and y(0);
62     x3y1 <= x(3) and y(1);
63     x3y2 <= x(3) and y(2);
64     x3y3 <= x(3) and y(3);
65
66     comp00: fa port map (a => x3y1, b => c01, sum => s00, cout => c00);
67     comp01: fa port map (a => x3y0, b => x2y1, cin => c02, sum => s01, cout => c01);
68     comp02: fa port map (a => x2y0, b => x1y1, cin => c03, sum => s02, cout => c02);
69     comp03: ha port map (a => x1y0, b => x0y1, sum => s03, cout => c03);
70     comp10: fa port map (a => c00, b => x3y2, cin => c11, sum => s10, cout => c10);
71     comp11: fa port map (a => s00, b => x2y2, cin => c12, sum => s11, cout => c11);
72     comp12: fa port map (a => s01, b => x1y2, cin => c13, sum => s12, cout => c12);
73     comp13: ha port map (a => s02, b => x0y2, sum => s13, cout => c13);
74     comp20: fa port map (a => c10, b => x3y3, cin => c21, sum => s20, cout => c20);
75     comp21: fa port map (a => s10, b => x2y3, cin => c22, sum => s21, cout => c21);
76     comp22: fa port map (a => s11, b => x1y3, cin => c23, sum => s22, cout => c22);
77     comp23: ha port map (a => s12, b => x0y3, sum => s23, cout => c23);
78
79     p(0) <= x(0) and y(0);
80     p(1) <= s03;
81     p(2) <= s13;
82     p(3) <= s23;
83     p(4) <= s22;

```

```

84 | p(5) <= s21;
85 | p(6) <= s20;
86 | p(7) <= c20;
87 |
88 | end Behavioral;

```

4x4 Multiplier Design (Test Bench Code)


```

1 | -----
2 | -- Engineer: Jose Luis Martinez
3 | --
4 | -- Create Date: 09/14/2020 09:33:16 AM
5 | -- Module Name: 4x4mult_tb - Behavioral
6 | -- Project Name: Computer Assignment 1
7 | -- Revision 0.01 - File Created
8 | -----
9 |
10 |
11 | library IEEE;
12 | use IEEE.STD_LOGIC_1164.ALL;
13 | use IEEE.NUMERIC_STD.ALL;
14 |
15 | entity mult4x4_tb is
16 | -- Port ( );
17 | end mult4x4_tb;
18 |
19 | architecture Behavioral of mult4x4_tb is
20 |
21 | signal x_tb : STD_LOGIC_VECTOR (3 downto 0);
22 | signal y_tb : STD_LOGIC_VECTOR (3 downto 0);
23 | signal p_tb : STD_LOGIC_VECTOR (7 downto 0);
24 |
25 | component mult4x4 is
26 |     Port ( x : in STD_LOGIC_VECTOR (3 downto 0);
27 |           y : in STD_LOGIC_VECTOR (3 downto 0);
28 |           p : out STD_LOGIC_VECTOR (7 downto 0));
29 | end component mult4x4;
30 |
31 | begin
32 |
33 | uut: mult4x4 port map ( x => x_tb,
34 |                        y => y_tb,
35 |                        p => p_tb);
36 |
37 | process
38 | begin
39 |
40 | for xFor in 0 to 15 loop
41 |     for yFor in 0 to 15 loop
42 |
43 |         x_tb <= std_logic_vector(to_unsigned(xFor, 4));
44 |         y_tb <= std_logic_vector(to_unsigned(yFor, 4));
45 |         wait for 10ns;
46 |     end loop;

```

```
46 end loop;  
47  
48 wait;  
49  
50 end process;  
51 end Behavioral;  
52
```

4x4 Multiplier Design (Waveforms)

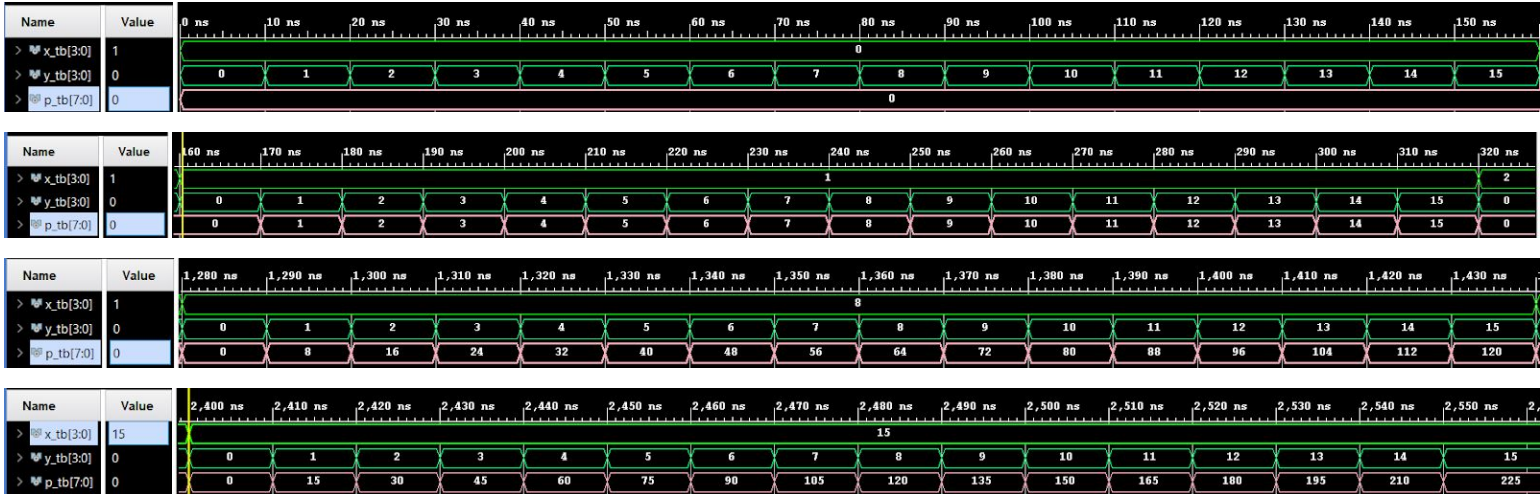

Part II:

Part II uses the half and full adder designs from above as well as the half and full subtractors below.

Half Subtractor Design (Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: hs - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13
14 entity hs is
15     Port ( a : in STD_LOGIC;
16           b : in STD_LOGIC;
17           bout : out STD_LOGIC;
18           diff : out STD_LOGIC);
19 end hs;
20
21 architecture Behavioral of hs is
22
23 begin
24
25     diff <= a xor b;
26     bout <= (not a) and b;
27
28 end Behavioral;
29
```

Half Subtractor Design (Test Bench Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: hs_tb - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12 use IEEE.NUMERIC_STD.ALL;
13
14 entity hs_tb is
15     -- Port ( );
16 end hs_tb;
```


Full Subtractor Design (Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: fs - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10
11
12  library IEEE;
13  use IEEE.STD_LOGIC_1164.ALL;
14
15  entity fs is
16      Port ( a : in STD_LOGIC;
17             b : in STD_LOGIC;
18             bin : in STD_LOGIC;
19             bout : out STD_LOGIC;
20             diff : out STD_LOGIC);
21  end fs;
22
23  architecture Behavioral of fs is
24
25  begin
26
27      diff <= (a xor b) xor bin;
28      bout <= ((not a) and b) or ((not(not a) xor (not b)) and bin);
29
30  end Behavioral;
31
```

Full Subtractor Design (Test Bench Code)


```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: fs_tb - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10  library IEEE;
11  use IEEE.STD_LOGIC_1164.ALL;
12  use IEEE.NUMERIC_STD.ALL;
13
```

```

13 :
14 entity fs_tb is
15     -- Port ( );
16 end fs_tb;
17
18 architecture Behavioral of fs_tb is
19
20     signal a_tb: std_logic;
21     signal b_tb: std_logic;
22     signal bin_tb: std_logic;
23     signal bout_tb: std_logic;
24     signal diff_tb: std_logic;
25
26 component fs is
27     Port ( a : in STD_LOGIC;
28           b : in STD_LOGIC;
29           bin : in STD_LOGIC;
30           bout : out STD_LOGIC;
31           diff : out STD_LOGIC);
32 end component fs;
33
34 begin
35
36 uut: fs port map ( a => a_tb,
37                   b => b_tb,
38                   bin => bin_tb,
39                   diff => diff_tb,
40                   bout => bout_tb);
41
42 process
43 begin
44
45 for aFor in 0 to 1 loop
46     for bFor in 0 to 1 loop
47         for binFor in 0 to 1 loop
48
49             if aFor = 1 then a_tb <= '1';
50             else a_tb <= '0';
51             end if;
52
53             if bFor = 1 then b_tb <= '1';
54
55             else b_tb <= '0';
56             end if;
57
58             if binFor = 1 then bin_tb <= '1';
59             else bin_tb <= '0';
60             end if;
61             wait for 325ns;
62         end loop;
63     end loop;
64 end loop;
65
66 end process;
67 end Behavioral;
68

```

Full Subtractor Design (Waveforms)

 

4x4 Signed Multiplier Design (Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: smult4x4 - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10 library IEEE;
11 use IEEE.STD_LOGIC_1164.ALL;
12
13 use IEEE.NUMERIC_STD.ALL;
14
15
16 entity smult3x3 is
17     Port ( x : in STD_LOGIC_VECTOR(3 downto 0);
18           y : in STD_LOGIC_VECTOR(3 downto 0);
19           p : out STD_LOGIC_VECTOR(7 downto 0));
20 end smult3x3;
21
22 architecture Behavioral of smult3x3 is
23
24 component ha is
25     Port ( a : in STD_LOGIC;
26           b : in STD_LOGIC;
27           sum : out STD_LOGIC;
28           cout : out STD_LOGIC);
29 end component ha;
30
31 component fa is
32     Port ( a : in STD_LOGIC;
33           b : in STD_LOGIC;
34           cin : in STD_LOGIC;
35           sum : out STD_LOGIC;
36           cout : out STD_LOGIC);
37 end component fa;
38
39 component hs is
40     Port ( a : in STD_LOGIC;
41           b : in STD_LOGIC;
```



```

42         bout : out STD_LOGIC;
43         diff : out STD_LOGIC);
44 end component hs;
45
46 component fs is
47     Port ( a : in STD_LOGIC;
48           b : in STD_LOGIC;
49           bin : in STD_LOGIC;
50           bout : out STD_LOGIC;
51           diff : out STD_LOGIC);
52 end component fs;
53
54 signal x0y0, x0y1, x0y2, x0y3: std_logic;
55 signal x1y0, x1y1, x1y2, x1y3: std_logic;
56 signal x2y0, x2y1, x2y2, x2y3: std_logic;
57 signal x3y0, x3y1, x3y2, x3y3: std_logic;
58
59 signal c00, c01, c02, c03, c04, c05, c06: std_logic;
60 signal c10, c11, c12, c13, c14, c15: std_logic;
61 signal d20, d21, d22, d23, d24: std_logic;
62
63 signal s00, s01, s02, s03, s04, s05, s06: std_logic;
64 signal s10, s11, s12, s13, s14, s15: std_logic;
65 signal b20, b21, b22, b23, b24: std_logic;
66
67 begin
68
69     x0y0 <= x(0) and y(0);
70     x0y1 <= x(0) and y(1);
71     x0y2 <= x(0) and y(2);
72     x0y3 <= x(0) and y(3);
73     x1y0 <= x(1) and y(0);
74     x1y1 <= x(1) and y(1);
75     x1y2 <= x(1) and y(2);
76     x1y3 <= x(1) and y(3);
77     x2y0 <= x(2) and y(0);
78     x2y1 <= x(2) and y(1);
79     x2y2 <= x(2) and y(2);
80     x2y3 <= x(2) and y(3);
81     x3y0 <= x(3) and y(0);
82     x3y1 <= x(3) and y(1);
83     x3y2 <= x(3) and y(2);
84     x3y3 <= x(3) and y(3);
85
86     comp00: ha port map (a => x1y0, b => x0y1, sum => s00, cout => c00);
87     comp01: fa port map (a => x2y0, b => x1y1, cin => c00, sum => s01, cout => c01);
88     comp02: fa port map (a => x3y0, b => x2y1, cin => c01, sum => s02, cout => c02);
89     comp03: fa port map (a => x3y0, b => x3y1, cin => c02, sum => s03, cout => c03);
90     comp04: fa port map (a => x3y0, b => x3y1, cin => c03, sum => s04, cout => c04);

```

```

91 comp05: fa port map (a => x3y0, b => x3y1, cin => c04, sum => s05, cout => c05);
92 comp06: fa port map (a => x3y0, b => x3y1, cin => c05, sum => s06, cout => c06);
93
94 comp10: ha port map (a => s01, b => x0y2, sum => s10, cout => c10);
95 comp11: fa port map (a => s02, b => x1y2, cin => c10, sum => s11, cout => c11);
96 comp12: fa port map (a => s03, b => x2y2, cin => c11, sum => s12, cout => c12);
97 comp13: fa port map (a => s04, b => x3y2, cin => c12, sum => s13, cout => c13);
98 comp14: fa port map (a => s05, b => x3y2, cin => c13, sum => s14, cout => c14);
99 comp15: fa port map (a => s06, b => x3y2, cin => c14, sum => s15, cout => c15);
100
101 comp20: hs port map (a => s11, b => x0y3, bout => b20, diff => d20);
102 comp21: fs port map (a => s12, b => x1y3, bin => b20, bout => b21, diff => d21);
103 comp22: fs port map (a => s13, b => x2y3, bin => b21, bout => b22, diff => d22);
104 comp23: fs port map (a => s14, b => x3y3, bin => b22, bout => b23, diff => d23);
105 comp24: fs port map (a => s15, b => x3y3, bin => b23, bout => b24, diff => d24);
106
107 p(0) <= x0y0;
108 p(1) <= s00;
109 p(2) <= s10;
110 p(3) <= d20;
111 p(4) <= d21;
112 p(5) <= d22;
113 p(6) <= d23;
114 p(7) <= d24;
115
116 end Behavioral;
117

```

4x4 Signed Multiplier Design (Test Bench Code)

```

1 -----
2 -- Engineer: Jose Luis Martinez
3 --
4 -- Create Date: 09/14/2020 09:33:16 AM
5 -- Module Name: 4x4smult_tb - Behavioral
6 -- Project Name: Computer Assignment 1
7 -- Revision 0.01 - File Created
8 -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity smult3x3_tb is
16 -- Port ( );
17 end smult3x3_tb;
18
19 architecture Behavioral of smult3x3_tb is
20
21 signal x_tb : STD_LOGIC_VECTOR (3 downto 0);

```

```

22 signal y_tb : STD_LOGIC_VECTOR (3 downto 0);
23 signal p_tb : STD_LOGIC_VECTOR (7 downto 0);
24
25 component smult3x3 is
26     Port ( x : in STD_LOGIC_VECTOR (3 downto 0);
27           y : in STD_LOGIC_VECTOR (3 downto 0);
28           p : out STD_LOGIC_VECTOR (7 downto 0));
29 end component smult3x3;
30
31 begin
32
33 uutttt: smult3x3 port map ( x => x_tb,
34                             y => y_tb,
35                             p => p_tb);
36
37 process
38 begin
39
40 for xFor in -8 to 7 loop
41     for yFor in -8 to 7 loop
42         x_tb <= std_logic_vector(to_signed(xFor, 4));
43         y_tb <= std_logic_vector(to_signed(yFor, 4));
44         wait for 10ns;
45     end loop;
46 end loop;
47
48 wait;
49
50 end process;
51 end Behavioral;
52

```

4x4 Signed Multiplier Design (Waveforms)

