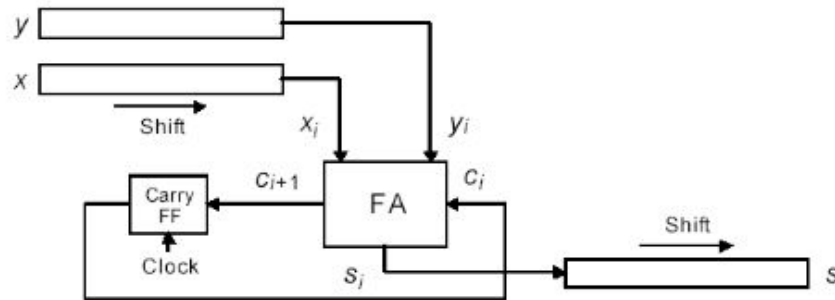


Fall 2020
California State University, Northridge
Department of Electrical and Computer Engineering
Computer Assignment 4:
Serial Adder

The following diagram shows the top level block diagram of a synchronous serial adder. All the inputs and outputs are shown. The circuit consists of two serial data inputs: x and y , system clock, system reset, and a serial output data s , all single bits. Serial data are synchronized with clock and the ordering of bits on serial input streams is from LSB applied first to MSB applied last.



1. Write a structural code for the top level of the above serial adder. The lower level modules such as carry flip flop, shift registers, and full adder must be modeled behaviorally. The following VHDL entity is given for your reference. You should not use any port other than what is given here. **(25 points)**

```
entity sadder
port (x, y, clk, reset:      in std_logic;
      s:                    out std_logic);
end entity;
```

Your structural model must instantiate the lower level modules such as shift register, full adder, and single D flip flop. Write a parameterized VHDL model for serial input serial output register and instantiate it in your design three times for x , y , and s registers. **(10 points)**

Serial Adder (Top Level Design Code)

```
1  -----
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: Serial Adder Design
7  --
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity serialAdder is
16     Port (
17         x, y, clk, rst, start: in std_logic;
18         s: out std_logic);
19 end serialAdder;
20
21 architecture Behavioral of serialAdder is
22
23     component fa is
24         Port (
25             A: in std_logic;
26             B: in std_logic;
27             cin: in std_logic;
28             sum: out std_logic;
29             cout: out std_logic);
30     end component fa;
31
32     component shiftRegister is
33         Port (
34             D, clk, rst: in std_logic;
35             Q: out std_logic);
36     end component shiftRegister;
37
38     component dff is
39         Port (
40             D, clk, rst: in std_logic;
41             Q: out std_logic);
42     end component dff;
43
44     signal Yi, Xi, Ci, Co, Si: std_logic;
45     begin
46
47     coutDff: dff port map(D => Co, clk => clk, rst => rst, Q => Ci);
48     Adder: fa port map(A => Xi, B => Yi, cin => Ci, sum => Si, cout => Co);
```

```
49 XSISO: shiftRegister port map(D => x, clk => clk, rst => rst, Q => Xi);
50 YSISO: shiftRegister port map(D => y, clk => clk, rst => rst, Q => Yi);
51 SSISO: shiftRegister port map(D => Si, clk => clk, rst => rst, Q => s);
52
53 end Behavioral;
54
```

Full Adder (Design Code)

```
1  -----
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: Full Adder Design
7  --
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity fa is
16     Port (
17         A: in std_logic;
18         B: in std_logic;
19         cin: in std_logic;
20         sum: out std_logic;
21         cout: out std_logic);
22 end fa;
23
24 architecture Behavioral of fa is
25
26 begin
27
28     sum <= A xor B xor cin;
29     cout <= (A or B) and (A or cin) and (B or cin);
30
31 end Behavioral;
32
```

D-FF (Design Code)

```
1  -----
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: D-Flip-Flop Design
7  --
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity dff is
16     Port (
17         D, clk, rst: in std_logic;
18         Q: out std_logic);
19 end dff;
20
21 architecture Behavioral of dff is
22
23     begin
24
25     process(clk, rst)
26     begin
27         if rst = '1' then
28             Q <= '0';
29         elsif rising_edge(clk) then
30             Q <= D;
31         end if;
32     end process;
33
34 end Behavioral;
35
```

Shift Register (Design Code)

```
1  -----
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: Shift Register Design
7  --
8  -----
9
10
11 library IEEE;
```

```
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity shiftRegister is
16     generic (WIDTH: integer := 16);
17     Port (
18         D, clk, rst: in std_logic;
19         Q: out std_logic);
20 end shiftRegister;
21
22 architecture Behavioral of shiftRegister is
23
24     signal tmp_Signal: std_logic_vector(WIDTH-1 downto 0);
25     begin
26
27     process(clk, rst)
28     begin
29
30         if (rst = '1') then
31             tmp_signal <= (others => '0');
32         elsif rising_edge(clk) then
33             for i in 0 to WIDTH-2 loop
34                 tmp_signal(i+1) <= tmp_signal(i);
35             end loop;
36             tmp_signal(0) <= D;
37         end if;
38     end process;
39
40     Q <= tmp_signal(WIDTH-1);
41
42 end Behavioral;
43
```

Serial Adder (Test Bench)

```
1 -----
2 --
3 -- Engineer: Jose L. Martinez
4 --
5 -- Create Date: 11/07/2020 10:14:54 PM
6 -- Design Name: Serial Adder Test Bench
7 --
8 -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
```



```
14
15 entity serialAdder_tb is
16 end serialAdder_tb;
17
18 architecture Behavioral of serialAdder_tb is
19
20 component serialAdder is
21     Port (
22         x, y, clk, rst: in std_logic;
23         s: out std_logic);
24 end component serialAdder;
25
26     signal x_tb, y_tb, clk_tb, rst_tb: std_logic;
27     signal s_tb: std_logic;
28     constant CP: time := 10 ns;
29
30 begin
31
32     testSA: serialAdder port map(x => x_tb, y => y_tb, clk => clk_tb, rst => rst_tb, s => s_tb);
33
34 process
35 begin
36     clk_tb <= '1';
37     wait for CP/2;
38     clk_tb <= '0';
39     wait for CP/2;
40 end process;
41
42 process
43 begin
44     rst_tb <= '1';
45     wait for CP;
46     rst_tb <= '0';
47     wait;
48 end process;
49
50 process
51 begin
52     x_tb <= '0';
53     y_tb <= '0';
54     wait for CP;
55     x_tb <= '0';
56     y_tb <= '1';
57     wait for CP;
58     x_tb <= '1';
59     y_tb <= '1';
60     wait for CP;
61     x_tb <= '1';
62     y_tb <= '1';
63     wait for CP;
64     x_tb <= '0';
65     y_tb <= '1'; --
```

```
66 ○ wait for CP;
67 ○ x_tb <= '1';
68 ○ y_tb <= '1';
69 ○ wait for CP;
70 ○ x_tb <= '1';
71 ○ y_tb <= '1';
72 ○ wait for CP;
73 ○ x_tb <= '1';
74 ○ y_tb <= '0';
75 ○ wait for CP;
76 ○ x_tb <= '1';
77 ○ y_tb <= '0'; --
78 ○ wait for CP;
79 ○ x_tb <= '0';
80 ○ y_tb <= '0';
81 ○ wait for CP;
82 ○ x_tb <= '0';
83 ○ y_tb <= '0';
84 ○ wait for CP;
85 ○ x_tb <= '0';
86 ○ y_tb <= '0';
87 ○ wait for CP;
88 ○ x_tb <= '0';
89 ○ y_tb <= '0'; --
90 ○ wait for CP;
91 ○ x_tb <= '0';
92 ○ y_tb <= '0';
93 ○ wait for CP;
94 ○ x_tb <= '1';
95 ○ y_tb <= '1';
96 ○ wait for CP;
97 ○ x_tb <= '0';
98 ○ y_tb <= '0';
99 ○ wait for CP;
100 ○ x_tb <= '1';
101 ○ y_tb <= '1'; --
102 ○ wait for CP;
103 ○ x_tb <= '0';
104 ○ y_tb <= '0';
105 ○ wait;
106 ○ end process;
107
108 ○ end Behavioral;
109
```

Serial Adder (Waveforms)



2. The block diagram shown above does not indicate the start/end of serial data on the input/output. Assume this serial adder is used to add 16 bits of serial data at a time. Another input called START for the duration of 16 clock pulses indicates the LSB bit of the serial data. Modify your design to start adding the bits serially when START pulse is active. START bit is active for only one clock pulse. When START is enabled for one clock cycle, your circuit should start adding the next 16 bits serially and then stop until the next pulse. **(25 points)**

Serial Adder With Start (Waveforms)

```

1  --
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: Serial Adder Design
7  --
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity serialAdder is
16     Port (
17         x, y, clk, rst, start: in std_logic;
18         s, max: out std_logic);
19 end serialAdder;
20
21 architecture Behavioral of serialAdder is
22
23     component fa is
24         Port (
25             A: in std_logic;
26             B: in std_logic;
27             cin: in std_logic;
28             sum: out std_logic;
29             cout: out std_logic);
30     end component fa;
31
32     component shiftRegister is
33         Port (
34             D, clk, rst: in std_logic;
35             Q: out std_logic);
36     end component shiftRegister;
37
38     component dff is
39         Port (
40             D, clk, rst: in std_logic;
41             Q: out std_logic);

```



```
42 end component dff;
43
44 signal Yi, Xi, Ci, Co, Si: std_logic;
45 signal enabled, clkEnabled: std_logic;
46 signal count: unsigned(5 downto 0);
47
48 begin
49
50   clkEnabled <= enabled and clk;
51
52   coutDff: dff port map(D => Co, clk => clkEnabled, rst => rst, Q => Ci);
53   Adder: fa port map(A => Xi, B => Yi, cin => Ci, sum => Si, cout => Co);
54   XSISO: shiftRegister port map(D => x, clk => clkEnabled, rst => rst, Q => Xi);
55   YSISO: shiftRegister port map(D => y, clk => clkEnabled, rst => rst, Q => Yi);
56   SSISO: shiftRegister port map(D => Si, clk => clkEnabled, rst => rst, Q => s);
57
58   process(clk)
59   begin
60     if start = '1' then
61       count <= (others => '0');
62       enabled <= '1';
63       max <= '0';
64     elsif count = to_unsigned(48, 6) then
65       max <= '1';
66       enabled <= '0';
67     elsif rising_edge(clk) then
68       count <= count + "0001";
69     end if;
70   end process;
71
72 end Behavioral;
```

3. Write a VHDL test bench for the serial adder design and show the correct functionality of your design for part 2. Your design must test a real case of $x = 0xA0F6$ and $y = 0xA03F$. What is the result in hex format? Does this operation create overflow if these inputs are signed? Does it create overflow if these inputs are unsigned? **(40 points)**

D-Flip-Flop (Test Bench)


```
1  --
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: D-Flip-Flop Test Bench
7  --
8  --
9  --
10 --
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15
16 entity dff_tb is
17     -- Port ( );
18 end dff_tb;
19
20 architecture Behavioral of dff_tb is
21
22     component dff is
23         Port (
24             D, clk, rst: in std_logic;
25             Q: out std_logic);
26 end component dff;
27
28 signal D_tb, clk_tb, rst_tb, Q_tb: std_logic;
29 constant CP: time := 10 ns;
30
31 begin
32
```

```

33 testDff: dff port map(D => D_tb, clk => clk_tb, rst => rst_tb, Q => Q_tb);
34
35 process
36 begin
37   clk_tb <= '1';
38   wait for CP/2;
39   clk_tb <= '0';
40   wait for CP/2;
41 end process;
42
43 process
44 begin
45   D_tb <= '0';
46   rst_tb <= '0';
47   wait for CP;
48   D_tb <= '1';
49   rst_tb <= '0';
50   wait for CP;
51   D_tb <= '0';
52   rst_tb <= '1';
53   wait for CP;
54   D_tb <= '1';
55   rst_tb <= '1';
56   wait for CP;
57 end process;
58
59 end Behavioral;
60

```

D-Flip-Flop (Waveforms)

 

Full Adder (Test Bench)


```

1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 09/14/2020 09:33:16 AM
5  -- Module Name: fa_tb - Behavioral
6  -- Project Name: Computer Assignment 1
7  -- Revision 0.01 - File Created
8  -----
9
10
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity fas_tb is

```

```
16  -- Port ( );
17  end fas_tb;
18
19  architecture Behavioral of fas_tb is
20
21      signal a_tb: std_logic;
22      signal b_tb: std_logic;
23      signal cin_tb: std_logic;
24      signal sum_tb: std_logic;
25      signal cout_tb: std_logic;
26
27  component fa is
28      Port ( a : in STD_LOGIC;
29            b : in STD_LOGIC;
30            cin : in STD_LOGIC;
31            sum : out STD_LOGIC;
32            cout : out STD_LOGIC);
33  end component fa;
34
35  begin
36
37  uut: fa port map ( a => a_tb,
38                    b => b_tb,
39                    cin => cin_tb,
40                    sum => sum_tb,
41                    cout => cout_tb);
42
43  process
44  begin
45
46  for aFor in 0 to 1 loop
47      for bFor in 0 to 1 loop
48          for cinFor in 0 to 1 loop
49
50              if aFor = 1 then a_tb <= '1';
51              else a_tb <= '0';
52              end if;
53
54              if bFor = 1 then b_tb <= '1';
55              else b_tb <= '0';
56              end if;
57
58              if cinFor = 1 then cin_tb <= '1';
59              else cin_tb <= '0';
60              end if;
61              wait for 325ns;
62
63          end loop;
64      end loop;
65  end loop;
66
67  end process;
68  end Behavioral;
```

Full Adder (Waveforms)

 

SISO (Test Bench)

```

1  --
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: Shift Register Test Bench
7  --
8  --
9  --
10 --
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14
15 entity shiftRegister_tb is
16   -- Port ( );
17 end shiftRegister_tb;
18
19 architecture Behavioral of shiftRegister_tb is
20
21   component shiftRegister is
22     generic (WIDTH: integer := 16);
23     Port (
24       D, clk, rst: in std_logic;
25       Q: out std_logic);
26   end component shiftRegister;
27
28   signal D_tb, clk_tb, rst_tb, Q_tb: std_logic;
29   constant CP: time := 10 ns;
30
31   begin
32
33     SISOTEST: shiftRegister port map(D => D_tb, clk => clk_tb, rst => rst_tb, Q => Q_tb);
34
35   process
36   begin
37     clk_tb <= '1';
38     wait for CP/2;
39     clk_tb <= '0';
40     wait for CP/2;
41   end process;
42


```



```

42
43 process
44 begin
45   rst_tb <= '1';
46   wait for CP;
47   rst_tb <= '0';
48   wait;
49 end process;
50
51 process
52 begin
53   D_tb <= '0';
54   wait for CP;
55   D_tb <= '1';
56   wait for CP;
57   D_tb <= '1';
58   wait for CP;
59   D_tb <= '0';
60   wait for CP;
61   D_tb <= '0';
62   wait for CP;
63   D_tb <= '1';
64   wait for CP;
65   D_tb <= '0';
66   wait for CP;
67   D_tb <= '1';
68   wait for CP;
69   D_tb <= '0';
70   wait;
71 end process;
72
73 end Behavioral;
74
  
```

SISO (Waveforms)

 

Serial Adder With Start/End (Test Bench)

```
1  --
2  --
3  -- Engineer: Jose L. Martinez
4  --
5  -- Create Date: 11/07/2020 10:14:54 PM
6  -- Design Name: Serial Adder Test Bench
7  --
8  --
9  --
10 --
11 library IEEE;
12 use IEEE.STD_LOGIC_1164.ALL;
13 use IEEE.NUMERIC_STD.ALL;
14 --
15 entity serialAdder_tb is
16 end serialAdder_tb;
17 --
18 architecture Behavioral of serialAdder_tb is
19 --
20 component serialAdder is
21     Port (
22         x, y, clk, rst, start: in std_logic;
23         s, max: out std_logic);
24 end component serialAdder;
25 --
26 signal x_tb, y_tb, clk_tb, rst_tb, start_tb: std_logic;
27 signal s_tb, max_tb: std_logic;
28 constant CP: time := 10 ns;
29 --
30 begin
31 --
32 testSA: serialAdder port map(x => x_tb, y => y_tb, clk => clk_tb, rst => rst_tb, start => start_tb, s => s_tb, max => max_tb);
33 --
34 process
35 begin
36     clk_tb <= '1';
37     wait for CP/2;
38     clk_tb <= '0';
39     wait for CP/2;
40 end process;
41 --
42 process
43 begin
44     rst_tb <= '1';
45     wait for CP;
46     rst_tb <= '0';
47     wait;
48 end process;
49 --
50 process
51 begin
52     x_tb <= '0';
53     y_tb <= '0';
54     y_tb <= '0';
55     start_tb <= '1';
56     wait for CP;
57     start_tb <= '0';
58     x_tb <= '0';
59     y_tb <= '1';
60     wait for CP;
61     x_tb <= '1';
62     y_tb <= '1';
63     wait for CP;
64     x_tb <= '1';
65     y_tb <= '1';
66     wait for CP;
67     x_tb <= '0';
68     y_tb <= '1'; --
```

```
68 ○ wait for CP;
69 ○ x_tb <= '1';
70 ○ y_tb <= '1';
71 ○ wait for CP;
72 ○ x_tb <= '1';
73 ○ y_tb <= '1';
74 ○ wait for CP;
75 ○ x_tb <= '1';
76 ○ y_tb <= '0';
77 ○ wait for CP;
78 ○ x_tb <= '1';
79 ○ y_tb <= '0'; --
80 ○ wait for CP;
81 ○ x_tb <= '0';
82 ○ y_tb <= '0';
83 ○ wait for CP;
84 ○ x_tb <= '0';
85 ○ y_tb <= '0';
86 ○ wait for CP;
87 ○ x_tb <= '0';
88 ○ y_tb <= '0';
89 ○ wait for CP;
90 ○ x_tb <= '0';
91 ○ y_tb <= '0'; --
92 ○ wait for CP;
93 ○ x_tb <= '0';
94 ○ y_tb <= '0';
95 ○ wait for CP;
96 ○ x_tb <= '1';
97 ○ y_tb <= '1';
98 ○ wait for CP;
99 ○ x_tb <= '0';
100 ○ y_tb <= '0';
101 ○ wait for CP;
102 ○ x_tb <= '1';
103 ○ y_tb <= '1'; --
104 ○ wait for CP;
105 ○ x_tb <= '0';
106 ○ y_tb <= '0';
107 ○ wait;
108 ○ end process;
109
110 ○ end Behavioral;
111
```

Serial Adder With Start/End (Waveforms)

