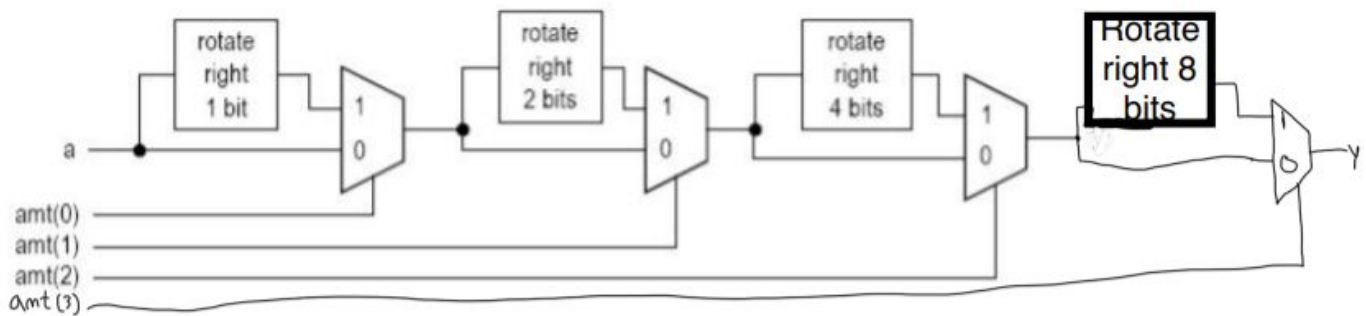


Fall 2020
California State University, Northridge
Department of Electrical and Computer Engineering
Computer Assignment 2: Design of a Combinational Barrel
Shifter/Rotator

1.) Expand the idea presented by this block diagram to design a 16 bit rotator and draw the block diagram.



2.) Design a 2x1 multiplexer using simple gates.

Stage 1 Multiplexer Design (Code)

```
1  -- Engineer: Jose Luis Martinez
2  --
3  -- Create Date: 10/10/2020 11:46:32 PM
4  -- Design Name: 16bit Barrel Shifter
5  -- Module Name: stage1MUX - Behavioral
6  -- Project Name: 16bit Barrel Shifter
7  -- Revision 0.01 - File Created
8  --
9  --
10
11
12
13  library IEEE;
14  use IEEE.STD_LOGIC_1164.ALL;
15
16  entity stage1MUX is
17      Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
```

```
18         sel: in STD_LOGIC;  
19         r: out STD_LOGIC_VECTOR(15 downto 0));  
20     end stage1MUX;  
21  
22     architecture Behavioral of stage1MUX is  
23  
24     begin  
25  
26         r <= (a(0) & a(15 downto 1)) when sel='1' else a;  
27  
28     end Behavioral;  
29
```

Stage 2 Multiplexer Design (Code)

```
1  -----  
2  -- Engineer: Jose Luis Martinez  
3  --  
4  -- Create Date: 10/10/2020 11:46:32 PM  
5  -- Design Name: 16bit Barrel Shifter  
6  -- Module Name: stage1MUX - Behavioral  
7  -- Project Name: 16bit Barrel Shifter  
8  -- Revision 0.01 - File Created  
9  --  
10 -----  
11  
12  
13 library IEEE;  
14 use IEEE.STD_LOGIC_1164.ALL;  
15  
16 entity stage1MUX is  
17     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);  
18           sel: in STD_LOGIC;  
19           r: out STD_LOGIC_VECTOR(15 downto 0));  
20 end stage1MUX;  
21  
22 architecture Behavioral of stage1MUX is  
23  
24     begin  
25  
26         r <= (a(0) & a(15 downto 1)) when sel='1' else a;  
27  
28     end Behavioral;  
29
```

Stage 3 Multiplexer Design (Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 10/10/2020 11:46:32 PM
5  -- Design Name: 16bit Barrel Shifter
6  -- Module Name: stage3MUX - Behavioral
7  -- Project Name: 16bit Barrel Shifter
8  -- Revision 0.01 - File Created
9  --
10 -----
11
12
13 library IEEE;
14 use IEEE.STD_LOGIC_1164.ALL;
15
16 entity stage3MUX is
17     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
18           sel: in STD_LOGIC;
19           r: out STD_LOGIC_VECTOR(15 downto 0));
20 end stage3MUX;
21
22 architecture Behavioral of stage3MUX is
23
24 begin
25
26 r <= (a(3 downto 0) & a(15 downto 4)) when sel='1' else a;
27
28 end Behavioral;
29
```

Stage 4 Multiplexer Design (Code)

```
1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 10/10/2020 11:46:32 PM
5  -- Design Name: 16bit Barrel Shifter
6  -- Module Name: stage4MUX - Behavioral
7  -- Project Name: 16bit Barrel Shifter
8  -- Revision 0.01 - File Created
9  --
10 -----
11
12
13 library IEEE;
```

```
14 use IEEE.STD_LOGIC_1164.ALL;
15
16 entity stage4MUX is
17     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
18           sel: in STD_LOGIC;
19           r: out STD_LOGIC_VECTOR(15 downto 0));
20 end stage4MUX;
21
22 architecture Behavioral of stage4MUX is
23
24 begin
25
26 r <= (a(7 downto 0) & a(15 downto 8)) when sel='1' else a;
27
28 end Behavioral;
29
```

3.) Instantiate the multiplexer in the top level design as many times as necessary to design a combinational rotator of length 16 bits.

16 Bit Barrel Shifter Design (Code)

```
1  -- Engineer: Jose Luis Martinez
2  --
3  --
4  -- Create Date: 10/10/2020 11:46:32 PM
5  -- Design Name: 16bit Barrel Shifter
6  -- Module Name: Bshifter_16 - Behavioral
7  -- Project Name: 16bit Barrel Shifter
8  -- Revision 0.01 - File Created
9  --
10 -----
11
12
13
14 library IEEE;
15 use IEEE.STD_LOGIC_1164.ALL;
16 use IEEE.NUMERIC_STD.ALL;
17
18 entity Bshifter_16 is
19     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
20           amt: in STD_LOGIC_VECTOR(3 downto 0);
21           y: out STD_LOGIC_VECTOR(15 downto 0));
22 end Bshifter_16;
23
24 architecture Behavioral of Bshifter_16 is
25
26 component stage1MUX is
27     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
28           sel: in STD_LOGIC;
29           r: out STD_LOGIC_VECTOR(15 downto 0));
30 end component stage1MUX;
31
32 component stage2MUX is
```

```
33     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);  
34           sel: in STD_LOGIC;  
35           r: out STD_LOGIC_VECTOR(15 downto 0));  
36 end component stage2MUX;  
37  
38 component stage3MUX is  
39     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);  
40           sel: in STD_LOGIC;  
41           r: out STD_LOGIC_VECTOR(15 downto 0));  
42 end component stage3MUX;  
43  
44 component stage4MUX is  
45     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);  
46           sel: in STD_LOGIC;  
47           r: out STD_LOGIC_VECTOR(15 downto 0));  
48 end component stage4MUX;  
49  
50 signal a1: std_logic_vector(15 downto 0);  
51 signal sel1, sel2, sel3, sel4: std_logic;  
52 signal r1, r2, r3, r4: std_logic_vector(15 downto 0);  
53  
54 begin  
55  
56 a1 <= a;  
57 sel1 <= amt(0);  
58 sel2 <= amt(1);  
59 sel3 <= amt(2);  
60 sel4 <= amt(3);  
61  
62 stage1: stage1MUX port map (a => a1, sel => sel1, r => r1);  
63 stage2: stage2MUX port map (a => r1, sel => sel2, r => r2);  
64 stage3: stage3MUX port map (a => r2, sel => sel3, r => r3);  
65 stage4: stage4MUX port map (a => r3, sel => sel4, r => r4);  
66  
67 y <= r4;  
68  
69 end Behavioral;  
70
```

4.) Simulate your design for the correct functionality. Write testbenches for 2x1 multiplexer as well as 16 bit combinational rotator.

Stage 1 Multiplexer Design (Test Bench Code)

```
1  -----  
2  -- Engineer: Jose Luis Martinez  
3  --  
4  -- Create Date: 10/10/2020 11:46:32 PM  
5  -- Design Name: 16bit Barrel Shifter  
6  -- Module Name: stage1MUX_tb - Behavioral  
7  -- Project Name: 16bit Barrel Shifter  
8  -- Revision 0.01 - File Created  
9  --  
10 -----
```




```
13 library IEEE;
14 use IEEE.STD_LOGIC_1164.ALL;
15 use IEEE.NUMERIC_STD.ALL;
16
17 entity stage1MUX_tb is
18     -- Port ( );
19 end stage1MUX_tb;
20
21 architecture Behavioral of stage1MUX_tb is
22
23     signal a_tb: STD_LOGIC_VECTOR(15 downto 0);
24     signal sel_tb: STD_LOGIC;
25     signal r_tb: STD_LOGIC_VECTOR(15 downto 0);
26
27     component stage1MUX is
28         Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
29               sel: in STD_LOGIC;
30               r: out STD_LOGIC_VECTOR(15 downto 0));
31     end component stage1MUX;
32
33     begin
34
35     stage1MUXsim: stage1MUX port map ( a => a_tb,
36                                       sel => sel_tb,
37                                       r => r_tb);
38
39     process
40     begin
41
42         a_tb <= b"0100_0000_1100_0000";
43         sel_tb <= '0';
44         wait for 125ns;
45
46         a_tb <= b"0100_0000_1100_0000";
47         sel_tb <= '1';
48         wait for 125ns;
49
50         a_tb <= b"0100_1111_0000_0000";
51         sel_tb <= '0';
52         wait for 125ns;
53
54         a_tb <= b"0100_1111_0000_0000";
55         sel_tb <= '1';
56         wait for 125ns;
57
58         a_tb <= b"0100_0000_0000_0001";
59         sel_tb <= '0';
60         wait for 125ns;
```

```

61
62   ○ a_tb <= b"0100_0000_0000_0001";
63   ○ sel_tb <= '1';
64   ○ wait for 125ns;
65
66   ○ a_tb <= b"1000_1001_1010_1011";
67   ○ sel_tb <= '0';
68   ○ wait for 125ns;
69
70   ○ a_tb <= b"1000_1001_1010_1011";
71   ○ sel_tb <= '1';
72   ○ wait for 125ns;
73
74   end process;
75
76   end Behavioral;
77
  
```

Stage 1 Multiplexer Design (Waveforms)

 

Stage 2 Multiplexer Design (Test Bench Code)

```

1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 10/10/2020 11:46:32 PM
5  -- Design Name: 16bit Barrel Shifter
6  -- Module Name: stage2MUX_tb - Behavioral
7  -- Project Name: 16bit Barrel Shifter
8  -- Revision 0.01 - File Created
9  --
10 -----
11
12
13 library IEEE;
14 use IEEE.STD_LOGIC_1164.ALL;
15 use IEEE.NUMERIC_STD.ALL;
16
17 entity stage2MUX_tb is
18   -- Port ( );
19 end stage2MUX_tb;
20
21 architecture Behavioral of stage2MUX_tb is
22
23   signal a_tb: STD_LOGIC_VECTOR(15 downto 0);
24   signal sel_tb: STD_LOGIC;
25   signal r_tb: STD_LOGIC_VECTOR(15 downto 0);
  
```

```
26 :
27 : component stage2MUX is
28 :     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
29 :           sel: in STD_LOGIC;
30 :           r: out STD_LOGIC_VECTOR(15 downto 0));
31 : end component stage2MUX;
32 :
33 : begin
34 :
35 : stage1MUXsim: stage2MUX port map ( a => a_tb,
36 :                                   sel => sel_tb,
37 :                                   r => r_tb);
38 :
39 : process
40 : begin
41 :
42 : ○ a_tb <= b"0100_0000_1100_0000";
43 : ○ sel_tb <= '0';
44 : ○ wait for 125ns;
45 :
46 : ○ a_tb <= b"0100_0000_1100_0000";
47 : ○ sel_tb <= '1';
48 : ○ wait for 125ns;
49 :
50 : ○ a_tb <= b"0100_1111_0000_0000";
51 : ○ sel_tb <= '0';
52 : ○ wait for 125ns;
53 :
54 : ○ a_tb <= b"0100_1111_0000_0000";
55 : ○ sel_tb <= '1';
56 : ○ wait for 125ns;
57 :
58 : ○ a_tb <= b"0100_0000_0000_0001";
59 : ○ sel_tb <= '0';
60 : ○ wait for 125ns;
61 :
62 : ○ a_tb <= b"0100_0000_0000_0001";
63 : ○ sel_tb <= '1';
64 : ○ wait for 125ns;
65 :
66 : ○ a_tb <= b"1000_1001_1010_1011";
67 : ○ sel_tb <= '0';
68 : ○ wait for 125ns;
69 :
70 : ○ a_tb <= b"1000_1001_1010_1011";
71 : ○ sel_tb <= '1';
72 : ○ wait for 125ns;
```




```

73
74 end process;
75
76 end Behavioral;
77

```

Stage 2 Multiplexer Design (Waveforms)

 

Stage 3 Multiplexer Design (Test Bench Code)

```


1
2
3
4
5
6
7
8
9
10
11
12
13 library IEEE;
14 use IEEE.STD_LOGIC_1164.ALL;
15 use IEEE.NUMERIC_STD.ALL;
16
17 entity stage3Mux_tb is
18   -- Port ( );
19 end stage3Mux_tb;
20
21 architecture Behavioral of stage3Mux_tb is
22
23   signal a_tb: STD_LOGIC_VECTOR(15 downto 0);
24   signal sel_tb: STD_LOGIC;
25   signal r_tb: STD_LOGIC_VECTOR(15 downto 0);
26
27   component stage3Mux is
28     Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
29           sel: in STD_LOGIC;
30           r: out STD_LOGIC_VECTOR(15 downto 0));
31   end component stage3Mux;
32
33   begin
34
35   stage3MUXsim: stage3Mux port map ( a => a_tb,
36                                     sel => sel_tb,
37                                     r => r_tb);
38
39   process
40   begin

```

```

41
42   ○ a_tb <= b"0100_0000_1100_0000";
43   ○ sel_tb <= '0';
44   ○ wait for 125ns;
45
46   ○ a_tb <= b"0100_0000_1100_0000";
47   ○ sel_tb <= '1';
48   ○ wait for 125ns;
49
50   ○ a_tb <= b"0100_1111_0000_0000";
51   ○ sel_tb <= '0';
52   ○ wait for 125ns;
53
54   ○ a_tb <= b"0100_1111_0000_0000";
55   ○ sel_tb <= '1';
56   ○ wait for 125ns;
57
58   ○ a_tb <= b"0100_0000_0000_0001";
59   ○ sel_tb <= '0';
60   ○ wait for 125ns;
61
62   ○ a_tb <= b"0100_0000_0000_0001";
63   ○ sel_tb <= '1';
64   ○ wait for 125ns;
65
66   ○ a_tb <= b"1000_1001_1010_1011";
67   ○ sel_tb <= '0';
68   ○ wait for 125ns;
69
70   ○ a_tb <= b"1000_1001_1010_1011";
71   ○ sel_tb <= '1';
72   ○ wait for 125ns;
73
74   ○ end process;
75
76   ○ end Behavioral;
77
  
```

Stage 3 Multiplexer Design (Waveforms)

 

Stage 4 Multiplexer Design (Test Bench Code)

```
1  -- Engineer: Jose Luis Martinez
2  --
3  --
4  -- Create Date: 10/10/2020 11:46:32 PM
5  -- Design Name: 16bit Barrel Shifter
6  -- Module Name: stage4MUX_tb - Behavioral
7  -- Project Name: 16bit Barrel Shifter
8  -- Revision 0.01 - File Created
9  --
10
11
12
13 library IEEE;
14 use IEEE.STD_LOGIC_1164.ALL;
15 use IEEE.NUMERIC_STD.ALL;
16
17 entity stage4MUX_tb is
18     -- Port ( );
19 end stage4MUX_tb;
20
21 architecture Behavioral of stage4MUX_tb is
22
23     signal a_tb: STD_LOGIC_VECTOR(15 downto 0);
24     signal sel_tb: STD_LOGIC;
25     signal r_tb: STD_LOGIC_VECTOR(15 downto 0);
26
27     component stage4MUX is
28         Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
29               sel: in STD_LOGIC;
30               r: out STD_LOGIC_VECTOR(15 downto 0));
31     end component stage4MUX;
32
33     begin
34
35     stage4MUXsim: stage4MUX port map ( a => a_tb,
36                                       sel => sel_tb,
37                                       r => r_tb);
38
39     process
40     begin
41
42     a_tb <= b"0100_0000_1100_0000";
43     sel_tb <= '0';
44     wait for 125ns;
45
46     a_tb <= b"0100_0000_1100_0000";
47     sel_tb <= '1';
48     wait for 125ns;
49
50     a_tb <= b"0100_1111_0000_0000";
51     sel_tb <= '0';
52     wait for 125ns;
53
54     a_tb <= b"0100_1111_0000_0000";
```

```

55   sel_tb <= '1';
56   wait for 125ns;
57
58   a_tb <= b"0100_0000_0000_0001";
59   sel_tb <= '0';
60   wait for 125ns;
61
62   a_tb <= b"0100_0000_0000_0001";
63   sel_tb <= '1';
64   wait for 125ns;
65
66   a_tb <= b"1000_1001_1010_1011";
67   sel_tb <= '0';
68   wait for 125ns;
69
70   a_tb <= b"1000_1001_1010_1011";
71   sel_tb <= '1';
72   wait for 125ns;
73
74   end process;
75
76   end Behavioral;
77

```

Stage 4 Multiplexer Design (Waveforms)



16 Bit Barrel Shifter Design (Test Bench Code)

```

1  -----
2  -- Engineer: Jose Luis Martinez
3  --
4  -- Create Date: 10/10/2020 11:46:32 PM
5  -- Design Name: 16bit Barrel Shifter
6  -- Module Name: Bshifter_16_tb - Behavioral
7  -- Project Name: 16bit Barrel Shifter
8  -- Revision 0.01 - File Created
9  --
10 -----
11
12
13
14 library IEEE;
15 use IEEE.STD_LOGIC_1164.ALL;
16 use IEEE.NUMERIC_STD.ALL;
17
18
19 entity Bshifter_16_tb is
20   -- Port ( );
21 end Bshifter_16_tb;
22

```

```

23  architecture Behavioral of Bshifter_16_tb is
24
25  signal a_tb: std_logic_vector(15 downto 0);
26  signal amt_tb: std_logic_vector(3 downto 0);
27  signal y_tb: std_logic_vector(15 downto 0);
28
29  component Bshifter_16 is
30      Port ( a: in STD_LOGIC_VECTOR(15 downto 0);
31            amt: in STD_LOGIC_VECTOR(3 downto 0);
32            y: out STD_LOGIC_VECTOR(15 downto 0));
33  end component Bshifter_16;
34
35  begin
36
37  Bshifter_16_SIM: Bshifter_16 port map (a => a_tb,
38                                         amt => amt_tb,
39                                         y => y_tb);
40
41  process
42
43      begin
44
45      a_tb <= b"0100_1111_0000_1111";
46      amt_tb <= "0001";
47      wait for 250ns;
48
49      amt_tb <= "1001";
50      wait for 250ns;
51
52      amt_tb <= "0110";
53      wait for 250ns;
54
55      amt_tb <= "1111";
56      wait for 250ns;
57  end process;
58
59  end Behavioral;
60

```

16 Bit Barrel Shifter Design (Waveforms)

